



# **DIGITAL DESIGN AND COMPUTER ORGANIZATION**

## **Boolean Algebra and Boolean Function**

---

**Team DDCO**

**Department of Computer Science and Engineering**

**Mathematical function:** defines a relationship between an independent variable and a dependent variable. E.g.  $A = \pi r^2$

- Example: Parabola
- Domain and range are set of real numbers
- Specified on Cartesian Plane

**Boolean function:** A mathematical function whose arguments, as well as the function itself, assume values from a two-element set (usually  $\{0,1\}$ ).

**Boolean algebra**, is a mathematical system, defined with a set of elements, a set of operators, and a number of unproved axioms or postulates.

A **Boolean function** is a function whose domain and range are the set  $\{0, 1\}$ .

A Boolean function has:

- At least one Boolean variable
- At least one Boolean operator
- At least one input from the set  $\{0, 1\}$

It produces an output that is also a member of the set  $\{0, 1\}$


## Boolean Constants and Variables

- Inputs and outputs of Boolean function are from the set  $\{0, 1\}$ 
  - **0 and 1 are called Boolean constants**
- In general, inputs and outputs of mathematical functions are represented by variables (like  $y = x^2$ )
  - **Inputs and outputs of Boolean functions are called as Boolean variables (like a, b and y)**

Specified as a truth table:

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

Specified as a logic gate:

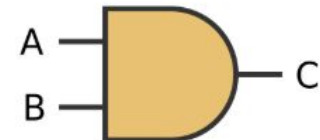



# Basic Logic Gates

Logic gates are **physical implementations of Boolean functions**.

A logic gate is a hardware component that performs a specific Boolean function.
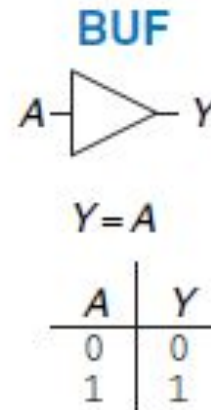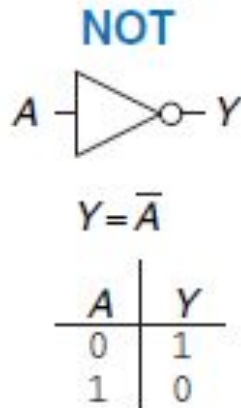
## Single Input Logic gates

The NOT gate's output is the inverse of its input




Buffer gate simply copies the input to the output.

# Basic Logic Gates

## Two-Input Logic Gates

AND

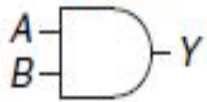

$$Y = AB$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

OR



$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

XOR



$$Y = A \oplus B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

NAND



$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


NOR



$$Y = \overline{A + B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

XNOR

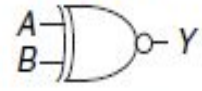


$$Y = \overline{A \oplus B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1


# Basic Logic Gates

## Multiple Input Logic Gates

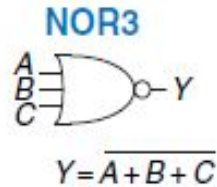

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

**Figure 1.20** Three-input NOR truth table

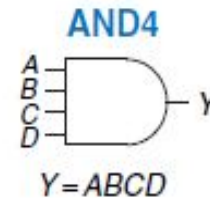


A	C	B	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

**Figure 1.22** Four-input AND truth table
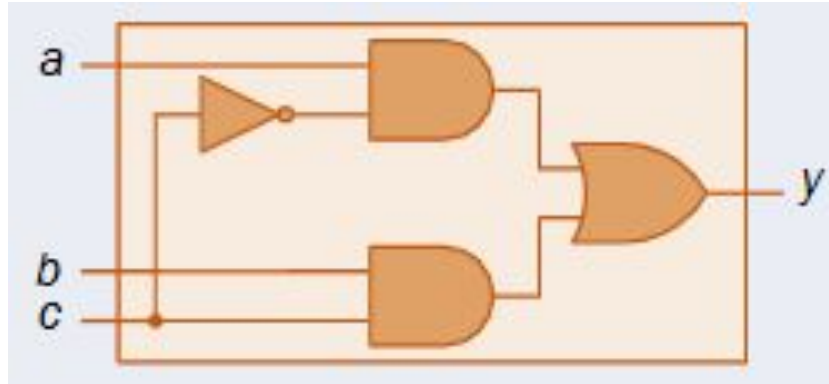
# What is a logic circuit?

Multiple logic gates combined together, with the output of one gate being connected to the input of another, form a ***logic circuit***.



A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1





# Logic Gates with Inverted Inputs



## Bubble

If a logic gate has a NOT gate on an input, the NOT gate can be replaced by a **bubble** on that input

## Bubble Example

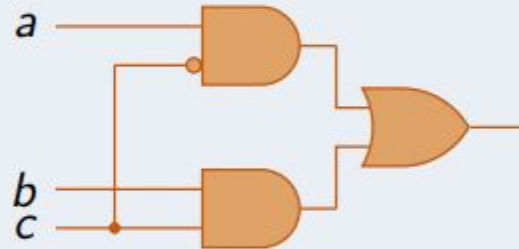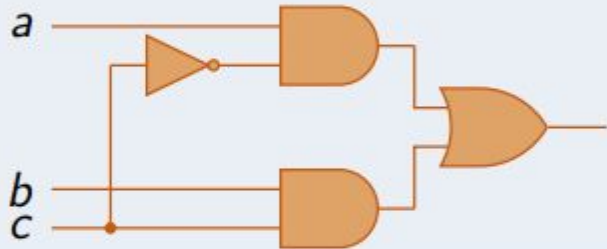

## Bubbled AND Example

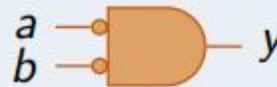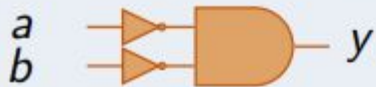

# Boolean Algebra(T1-Section 2.4)



## Algebra

In mathematics, an Algebra is composed of four things: a set of elements, operations on those elements, identity elements and laws/identities

### Standard Algebra

- **Set** Real numbers
- **Operations** Add, subtract, multiply, divide
- **Identity elements** 0 (for add), 1 (for multiply)
- **Laws/Identities** Commutative, associative, distributive, . . .

### Boolean Algebra

- **Set**  $\{0, 1\}$
- **Operations** AND, OR, NOT
- **Identity elements:** 1 (for AND), 0 (for OR)
- **Laws/Identities** Commutative, associative, distributive, . . .

# Boolean Laws

**Table 2.1**  
*Postulates and Theorems of Boolean Algebra*

Postulate 2	(a)	$x + 0 = x$	(b)	$x \cdot 1 = x$
Postulate 5	(a)	$x + x' = 1$	(b)	$x \cdot x' = 0$
Theorem 1	(a)	$x + x = x$	(b)	$x \cdot x = x$
Theorem 2	(a)	$x + 1 = 1$	(b)	$x \cdot 0 = 0$
Theorem 3, involution		$(x')' = x$		
Postulate 3, commutative	(a)	$x + y = y + x$	(b)	$xy = yx$
Theorem 4, associative	(a)	$x + (y + z) = (x + y) + z$	(b)	$x(yz) = (xy)z$
Postulate 4, distributive	(a)	$x(y + z) = xy + xz$	(b)	$x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a)	$(x + y)' = x'y'$	(b)	$(xy)' = x' + y'$
Theorem 6, absorption	(a)	$x + xy = x$	(b)	$x(x + y) = x$

**Useful Identity**  $a + \bar{a} \cdot b = a + b$   $a \cdot (\bar{a} + b) = a \cdot b$

# Boolean Laws

**THEOREM 1(a):**  $x + x = x$ .

Statement	Justification
$x + x = (x + x) \cdot 1$	postulate 2(b)
$= (x + x)(x + x')$	5(a)
$= x + xx'$	4(b)
$= x + 0$	5(b)
$= x$	2(a)

**THEOREM 1(b):**  $x \cdot x = x$ .

Statement	Justification
$x \cdot x = xx + 0$	postulate 2(a)
$= xx + xx'$	5(b)
$= x(x + x')$	4(a)
$= x \cdot 1$	5(a)
$= x$	2(b)

# Boolean Laws

**THEOREM 2(a):**  $x + 1 = 1$ .

Statement	Justification
$x + 1 = 1 \cdot (x + 1)$	postulate 2(b)
$= (x + x')(x + 1)$	5(a)
$= x + x' \cdot 1$	4(b)
$= x + x'$	2(b)
$= 1$	5(a)

**THEOREM 2(b):**  $x \cdot 0 = 0$ .

# Boolean Laws

Navigation icons: back, forward, search, etc.

**THEOREM 6(a):**  $x + xy = x$ .

**Statement**

$$\begin{aligned}x + xy &= x \cdot 1 + xy \\&= x(1 + y) \\&= x(y + 1) \\&= x \cdot 1 \\&= x\end{aligned}$$

**Justification**

postulate 2(b)  
4(a)  
3(a)  
2(a)  
2(b)

# Operator Precedence

---

The operator precedence for evaluating Boolean expressions is

- (1) parentheses,
- (2) NOT,
- (3) AND, and
- (4) OR.

In other words, expressions inside parentheses must be evaluated before all other operations. The next operation that holds precedence is the complement, and then follows the AND and, finally, the OR.

# Boolean Functions (T1- section 2.5)

---



Boolean function described by an **algebraic expression** consists of binary variables, the **constants 0 and 1**, and the logic operation symbols

A Boolean function expresses the **logical relationship** between binary variables and is evaluated by determining the binary value of the expression for all possible values of the variables.


**EX:**  $F_1 = x + y'z$

Value of  $F_1$  if  $x = 1$  or  $y = 0$  and  $z = 1$  ?



# Boolean Functions

A Boolean function can be transformed from an algebraic expression into a circuit diagram composed of logic gates connected in a particular structure.

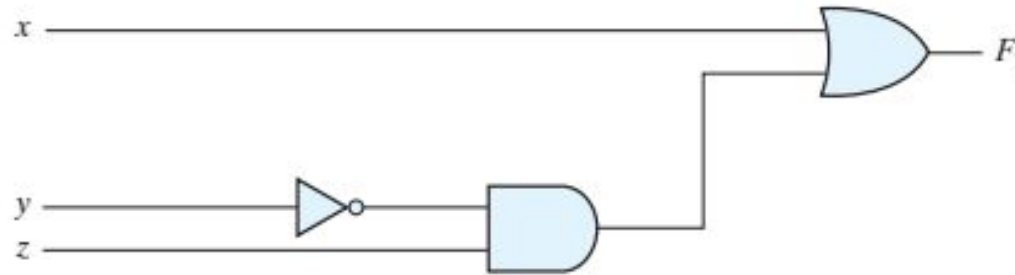

**FIGURE 2.1**

Gate implementation of  $F_1 = x + y'z$

# Boolean Functions

For  $N$  = Number of variables in the function:

- There exists  $2^N$  possible input combinations
- This results in  $2^N$  rows in the truth table
- Binary numbers counting from 0 through  $2^N - 1$
- So, there are  $2^{2^N}$  different truth tables for Boolean functions of  $N$  variables.
- $2^{2^N}$  different Boolean functions

$x$	$y$	$z$	$F_1$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

# Boolean Functions

---



**There is only one way that a Boolean function can be represented in a truth table.** However, when the function is in algebraic form, it can be expressed in a variety of ways, all of which have equivalent logic.

Boolean algebra, it is sometimes possible to obtain a simpler expression for the same function and thus reduce the number of gates in the circuit and the number of inputs to the gate.

**Designers are motivated to reduce the complexity and number of gates because their effort can significantly reduce the cost of a circuit.**

# Boolean Functions

---



*What is simplest form of below equation?*

$$F_2 = x'y'z + x'yz + xy'$$


# Boolean Functions

*What is simplest form of below equation?*


$$F_2 = x'y'z + x'yz + xy'$$

$$F_2 = x'y'z + x'yz + xy'$$
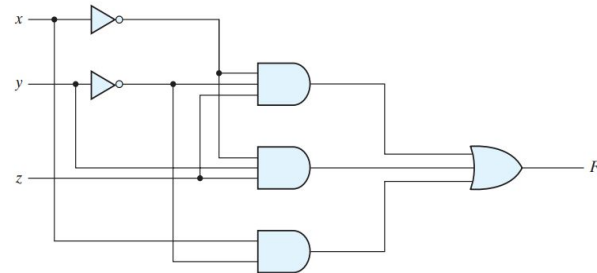
$$F_2 = x'y'z + x'yz + xy' = x'z(y' + y) + xy' = x'z + xy'$$



(a)  $F_2 = x'y'z + x'yz + xy'$

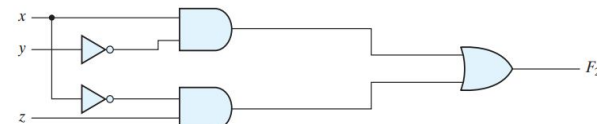

(b)  $F_2 = xy' + x'z$

**FIGURE 2.2**  
Implementation of Boolean function  $F_2$  with gates

# Questions

---

*Simplify the following Boolean expressions to a minimum number of literals:*

1.  $x(x' + y)$
2.  $x + x'y$
3.  $(x + y)(x + y')$
4.  $xy + x'z + yz$
5.  $(x + y)(x' + z)(y + z)$

# Questions

Simplify the following Boolean functions to a minimum number of literals.

1.  $x(x' + y) = xx' + xy = 0 + xy = xy.$

2.  $x + x'y = (x + x')(x + y) = 1(x + y) = x + y.$

3.  $(x + y)(x + y') = x + xy + xy' + yy' = x(1 + y + y') = x.$

4. 
$$\begin{aligned} xy + x'z + yz &= xy + x'z + yz(x + x') \\ &= xy + x'z + xyz + x'yz \\ &= xy(1 + z) + x'z(1 + y) \\ &= xy + x'z. \end{aligned}$$

5.  $(x + y)(x' + z)(y + z) = (x + y)(x' + z),$  by duality from function 4.

(4) and (5) are together known as consensus theorem.

# Complement of a Function

The complement of a function  $F$  is  $F'$  and is obtained from an interchange of 0's for 1's and 1's for 0's in the value of  $F$ . The complement of a function may be derived algebraically through DeMorgan's theorems.

$$\begin{aligned}(A + B + C)' &= (A + x)' && \text{let } B + C = x \\&= A'x' && \text{by theorem 5(a) (DeMorgan)} \\&= A'(B + C)' && \text{substitute } B + C = x \\&= A'(B'C') && \text{by theorem 5(a) (DeMorgan)} \\&= A'B'C' && \text{by theorem 4(b) (associative)}\end{aligned}$$



# Questions

---



*Find the complement of the functions  $F_1 = x'yz' + x'y'z$  and  $F_2 = x(y'z' + yz)$ .*

# Questions

***Find the complement of the functions  $F_1 = x'yz' + x'y'z$  and  $F_2 = x(y'z' + yz)$ .***

Find the complement of the functions  $F_1 = x'yz' + x'y'z$  and  $F_2 = x(y'z' + yz)$ . By applying DeMorgan's theorems as many times as necessary, the complements are obtained as follows:

$$\begin{aligned}F_1' &= (x'yz' + x'y'z)' = (x'yz')'(x'y'z)' = (x + y' + z)(x + y + z') \\F_2' &= [x(y'z' + yz)]' = x' + (y'z' + yz)' = x' + (y'z')'(yz)' \\&= x' + (y + z)(y' + z') \\&= x' + yz' + y'z\end{aligned}$$



A simpler procedure for deriving the complement of a function is to take the dual of the function and complement each literal. This method follows from the generalized forms of DeMorgan's theorems. Remember that the dual of a function is obtained from the interchange of AND and OR operators and 1's and 0's.

# Questions

---



*Find the complement of the functions  $F1 = x'yz' + x'y'z$  and  $F2 = x(y'z' + yz)$  taking their duals and complementing each literal.*

# Questions

*Find the complement of the functions  $F1 = x'yz' + x'y'z$  and  $F2 = x(y'z' + yz)$  taking their duals and complementing each literal.*

1.  $F_1 = x'yz' + x'y'z.$

The dual of  $F_1$  is  $(x' + y + z')(x' + y' + z).$

Complement each literal:  $(x + y' + z)(x + y + z') = F'_1.$

2.  $F_2 = x(y'z' + yz).$

The dual of  $F_2$  is  $x + (y' + z')(y + z).$

Complement each literal:  $x' + (y + z)(y' + z') = F'_2.$

# Boolean Formula

Each Boolean formula means a Boolean function as well as a logic circuit.


## Syntax Rules for Boolean Formulas

1. A Boolean constant (0 or 1) is a Boolean Formula
2. A Boolean variable (say  $x$ ) is a Boolean formula
3. If  $P$  and  $Q$  are Boolean formulas then so are:
  - a.  $(P \cdot Q)$
  - b.  $(P + Q)$
  - c.  $P'$
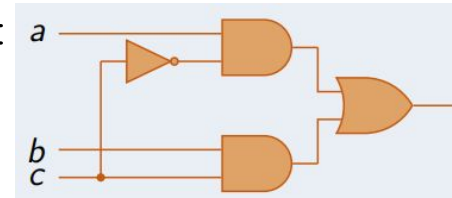
## Example of Boolean Formula: $((a \cdot c' + (b \cdot c))$

- From rule 2, Boolean variable  $a$  is a Boolean formula
- From rule 2, Boolean variable  $b$  is a Boolean formula
- From rule 2, Boolean variable  $c'$  is a Boolean formula
- From rule 3c and step (iii) above  $c'$ , is a Boolean formula
- From rule 3a, and steps (i) and (iv) above,  $(a \cdot c')$  is a Boolean formula
- From rule 3a, and steps (ii) and (iii) above,  $(b \cdot c)$  is a Boolean formula
- From rule 3b, and steps (v) and (vi) above,
- $((a \cdot c') + (b \cdot c))$  is a Boolean formula

The Boolean formula can be converted into a combinational logic circuit:



From Truth Table to Boolean Formula and its Minimization

- Given a combinational logic circuit or Boolean formula, we have learnt to construct its truth table
- **But, given a truth table, how to construct a Boolean formula (or combinational logic circuit) for it?**
- **Also, as there are multiple Boolean formulas / logic circuits for each truth table, how to pick the minimal one?**
- Above problem is called **logic minimization**
  - many metrics: smallest, fastest, least power consumption
  - our metric: smallest two level Sum of Products formula
  - may be more than one solution

# Questions

---

- *Consider Boolean functions of four inputs. What is the number of rows in the truth table of a four input Boolean function?*
- *What is the total number of Boolean functions of four inputs? Specify your answer as an integer.*

- *Consider Boolean functions of four inputs. What is the number of rows in the truth table of a four input Boolean function?*

A four-input Boolean function's truth table will have 16 rows. ( $2^4$ )

- *What is the total number of Boolean functions of four inputs? Specify your answer as an integer.*

There are  $2^{2^N}$  different Boolean functions on  $n$  Boolean variables

Here = 65536



# Questions

---

- *Is a logic gate. . .*
  - *A Boolean function? or*
  - *A digital electronic circuit?*

# Questions

---

- *Is a logic gate. . .*
  - *A Boolean function? or*
  - *A digital electronic circuit?*

It is both

This wonderful fact enables us to create the machines that perform mathematics, which we call computers.

# Questions

- *There are 16 different truth tables for Boolean functions of two variables. List each truth table. Give each one a short descriptive name (such as OR, NAND, and so on).*

A	B	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>	Y <sub>4</sub>	Y <sub>5</sub>	Y <sub>6</sub>	Y <sub>7</sub>	Y <sub>8</sub>	Y <sub>9</sub>	Y <sub>A</sub>	Y <sub>B</sub>	Y <sub>C</sub>	Y <sub>D</sub>	Y <sub>E</sub>	Y <sub>F</sub>
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

# Questions

- *There are 16 different truth tables for Boolean functions of two variables. List each truth table. Give each one a short descriptive name (such as OR, NAND, and so on).*

A	B	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>	Y <sub>4</sub>	Y <sub>5</sub>	Y <sub>6</sub>	Y <sub>7</sub>	Y <sub>8</sub>	Y <sub>9</sub>	Y <sub>A</sub>	Y <sub>B</sub>	Y <sub>C</sub>	Y <sub>D</sub>	Y <sub>E</sub>	Y <sub>F</sub>
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
		Zeros	NOR	A' B	NOT A	AB'	NOT B	XOR	NAND	AND	XNOR	B	A' +B	A	A+B'	OR	Ones

# Questions

---

- simplify the Boolean expression:

$$x(x' + y)$$

- A. 1
- B.  $x + y$
- C.  $x \cdot y$
- D.  $y$

# Questions

---

- simplify the Boolean expression:

$$x(x' + y)$$

- A. 1
- B.  $x + y$
- C.  $x \cdot y$
- D.  $y$

Ans: C



# THANK YOU

---

**Team DDCO**

**Department of Computer Science and Engineering**