



DIGITAL DESIGN AND COMPUTER ORGANIZATION

Mealy and Moore Models of FSMs

Team DDCO

Department of Computer Science and Engineering


Introduction(T1-section 5.5)



- The most general model of a sequential circuit has inputs, outputs, and internal states.
- It is customary to distinguish between two models of sequential circuits: the Mealy model and the Moore model.
- They differ only in the way the output is generated.


Block Diagrams

Mealy Machine

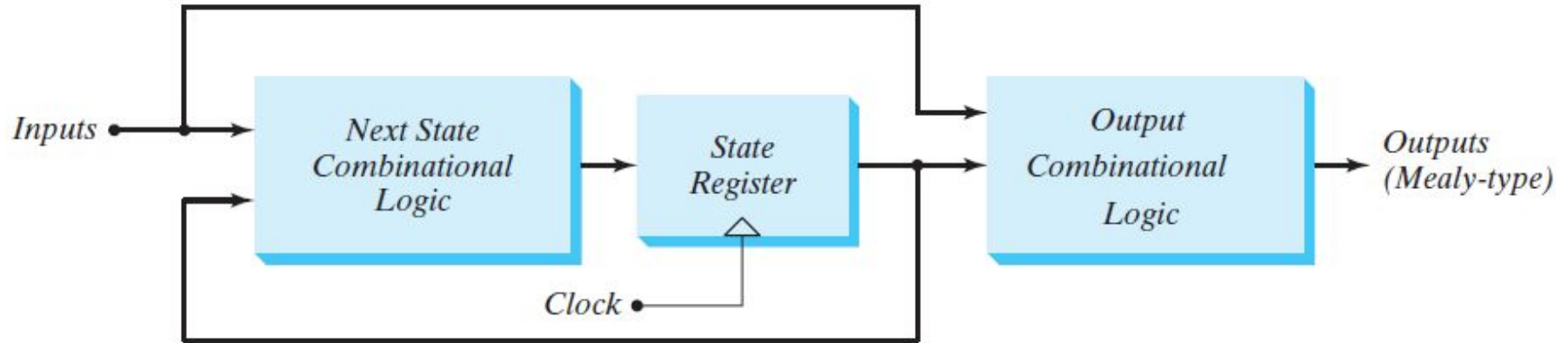

Block Diagrams


Moore Machine

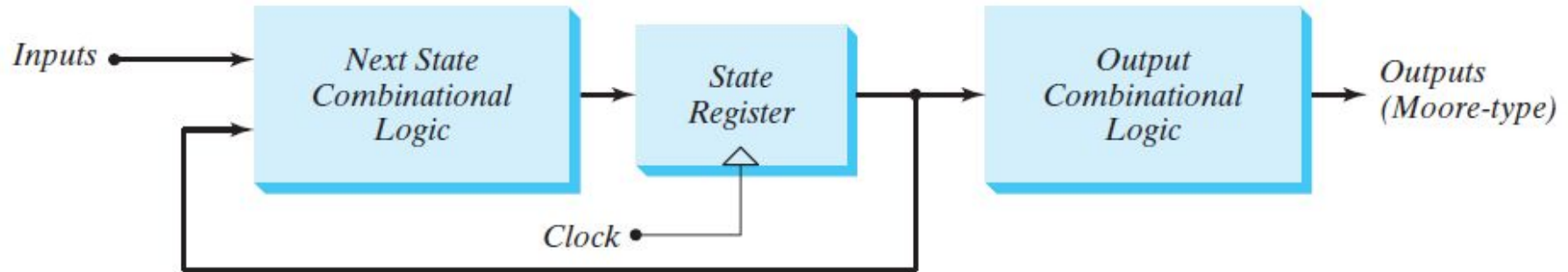

- In the Mealy model, the output is a function of both the present state and the input.
- In the Moore model, the output is a function of only the present state.
- A circuit may have both types of outputs.
- The two models of a sequential circuit are commonly referred to as a **finite state machine**, abbreviated FSM.
- The Mealy model of a sequential circuit is referred to as a Mealy FSM or Mealy machine.
- The Moore model is referred to as a Moore FSM or Moore machine.


Mealy Machine

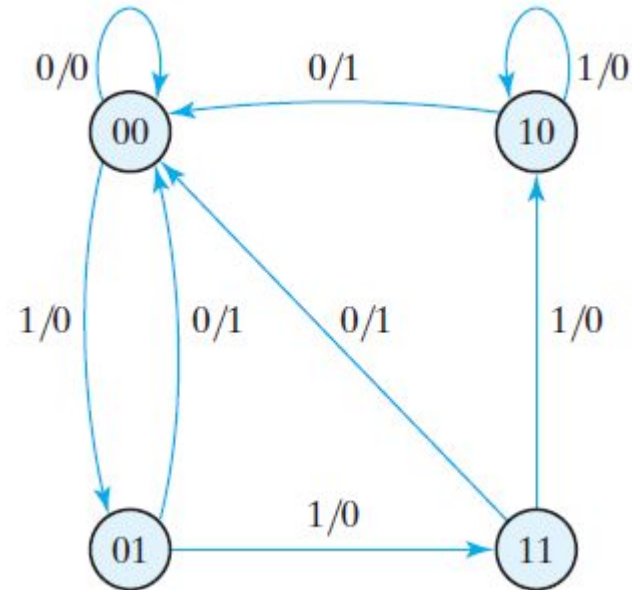- Output y is a function of both input x and the present state of A and B .
- The corresponding state diagram shows both the input and output values, separated by a slash along the directed lines between the states.




Moore Machine

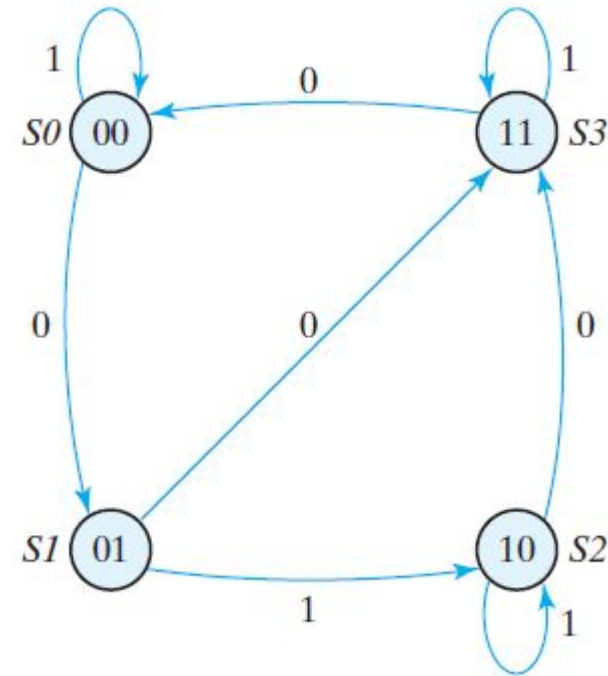- Here, the output is a function of the present state only.
- The corresponding state diagram has only inputs marked along the directed lines.
- The outputs are the flip-flop states marked inside the circles.



Moore Machine

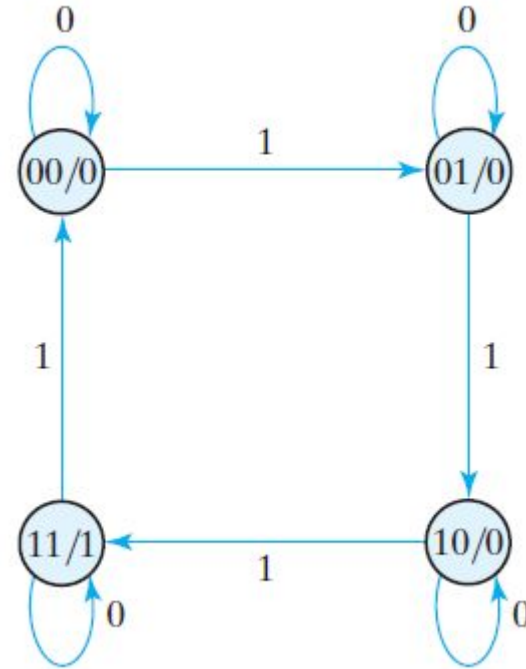- The output depends only on flip-flop values, and that makes it a function of the present state only.
- The input value in the state diagram is labeled along the directed line, but the output value is indicated inside the circle together with the present state.



Points to Remember

- **In a Moore model, the outputs of the sequential circuit are synchronized with the clock, because they depend only on flip-flop outputs that are synchronized with the clock.** In a Mealy model, the outputs may change if the inputs change during the clock cycle.
- In order to synchronize a Mealy-type circuit, the inputs of the sequential circuit must be synchronized with the clock and the outputs must be sampled immediately before the clock edge.
- The inputs are changed at the inactive edge of the clock to ensure that the inputs to the flip-flops stabilize before the active edge of the clock occurs.
- **Thus, the output of the Mealy machine is the value that is present immediately before the active edge of the clock.**

Mealy Model

Vending Machine with Coin Detection

- **How it works:** As soon as the correct coin is inserted (input) while the machine is in the “waiting” state, it immediately unlocks the product selection buttons (output).
- **Why Mealy:** Output depends on both **current state** (“waiting”) and **instant input** (coin detected) → faster interaction.

Moore Model

- **Example: Washing Machine Cycle**
- **How it works:** Once the washer enters the “spin” state, it spins for a fixed duration regardless of what buttons are pressed during that time.
- **Why Moore:** Output (motor spinning) depends only on **current state**, ensuring stability and avoiding mid-cycle changes

Moore:

- Needs separate states for “output=0” and “output=1.”
- More states.

Mealy:

- Can stay in one state and just make the output depend on x.
- Fewer states.

Consider a Mealy machine and a Moore machine implemented for the same problem. Which of the following is true?

- A) Moore machine always has fewer states.
- B) Mealy machine may have fewer states.
- C) Both have the same number of states always.
- D) Moore machine always produces output one clock earlier than Mealy.

Consider a Mealy machine and a Moore machine implemented for the same problem. Which of the following is true?

- A) Moore machine always has fewer states.
- B) Mealy machine may have fewer states.
- C) Both have the same number of states always.
- D) Moore machine always produces output one clock earlier than Mealy.

Answer: B — Mealy can have fewer states due to immediate output change.

In a Mealy machine, the output depends on:

- A) Present state only
- B) Present state and next state
- C) Present state and input
- D) Input only

The main difference between a Moore and a Mealy machine is that:

- A) Moore's output depends only on input.
- B) Mealy's output depends only on state.
- C) Moore's output depends only on state, while Mealy's output depends on state and input.
- D) Mealy's output is always faster than Moore's output, regardless of design.

In a Mealy machine, the output depends on:

- A) Present state only
- B) Present state and next state
- C) Present state and input
- D) Input only

Answer: C — Present state and input.

The main difference between a Moore and a Mealy machine is that:

- A) Moore's output depends only on input.
- B) Mealy's output depends only on state.
- C) Moore's output depends only on state, while Mealy's output depends on state and input.
- D) Mealy's output is always faster than Moore's output, regardless of design.

Answer: C — Moore → State only; Mealy → State + Input



THANK YOU

Team DDCO

Department of Computer Science and Engineering