

Digital Design and Computer Organisation Laboratory

3rd Semester, Academic Year 2025

Date:

Name: Dharani S	SRN: PES2UG24CS157	Section C
-----------------	-----------------------	--------------

Week Number: 2

1. Circuit- 1

Design.v

```
module simple_circuit (A, B, C, D, E);  
  output D, E;  input A, B, C;  wire w1;  
  and G1 (w1,A,B); // Optional gate instance name  
  not G2 (E,C);  
  or G3 ( D, w1 ,E);  
endmodule
```

Testbench.v

```

module tb_simple_circuit;
  wire D, E;
  reg A, B, C;

  simple_circuit M1(A, B, C, D, E);

  initial begin
    A = 1'b0; B = 1'b0; C = 1'b0; #20;
    A = 1'b0; B = 1'b0; C = 1'b1; #20;
    A = 1'b0; B = 1'b1; C = 1'b0; #20;
    A = 1'b0; B = 1'b1; C = 1'b1; #20;
    A = 1'b1; B = 1'b0; C = 1'b0; #20;
    A = 1'b1; B = 1'b0; C = 1'b1; #20;
    A = 1'b1; B = 1'b1; C = 1'b0; #20;
    A = 1'b1; B = 1'b1; C = 1'b1; #20;
  end

  initial begin
    $monitor($time, " A=%b, B=%b, C=%b, D=%b, E=%b", A, B, C, D, E);
  end

  initial begin
    $dumpfile("tb_simple_circuit.vcd");
    $dumpvars(1, tb_simple_circuit);
  end
endmodule

```


Vvp output:

```

PS C:\Users\anu29\Course_materials\sem3\DDCO_lab\week2\circuit1> vvp test
VCD info: dumpfile tb_simple_circuit.vcd opened for output.
      0 A=0, B=0, C=0, D=1, E=1
     20 A=0, B=0, C=1, D=0, E=0
     40 A=0, B=1, C=0, D=1, E=1
     60 A=0, B=1, C=1, D=0, E=0
     80 A=1, B=0, C=0, D=1, E=1
    100 A=1, B=0, C=1, D=0, E=0
    120 A=1, B=1, C=0, D=1, E=1
    140 A=1, B=1, C=1, D=1, E=0

```

Gtkwave:

 

2. Circuit- 2

Design.v

```
module simple_circuit (A, B, C, D);  
    output D;  
    input A, B, C;  
    wire w1;  
    and G1 (w1, C, B); // Optional gate instance name  
    or G3 (D, w1, A);  
endmodule
```

Testbench.v

```

module tb_simple_circuit;
  wire D;
  reg A, B, C;

  simple_circuit M1(A, B, C, D);

  initial begin
    A = 1'b0; B = 1'b0; C = 1'b0; #20;
    A = 1'b0; B = 1'b0; C = 1'b1; #20;
    A = 1'b0; B = 1'b1; C = 1'b0; #20;
    A = 1'b0; B = 1'b1; C = 1'b1; #20;
    A = 1'b1; B = 1'b0; C = 1'b0; #20;
    A = 1'b1; B = 1'b0; C = 1'b1; #20;
    A = 1'b1; B = 1'b1; C = 1'b0; #20;
    A = 1'b1; B = 1'b1; C = 1'b1; #20;
  end

  initial begin
    $monitor($time, " A=%b, B=%b, C=%b, D=%b", A, B, C, D);
  end

  initial begin
    $dumpfile("tb_simple_circuit.vcd");
    $dumpvars(1, tb_simple_circuit);
  end
endmodule

```


Vvp o/p:

```

PS C:\Users\anu29\Course_materials\sem3\DDCO_lab\week2\circuit2> vvp test
VCD info: dumpfile tb_simple_circuit.vcd opened for output.
      0 A=0, B=0, C=0, D=0
     20 A=0, B=0, C=1, D=0
     40 A=0, B=1, C=0, D=0
     60 A=0, B=1, C=1, D=1
     80 A=1, B=0, C=0, D=1
    100 A=1, B=0, C=1, D=1
    120 A=1, B=1, C=0, D=1
    140 A=1, B=1, C=1, D=1

```

Gtkwave:

 

Circuit 3:

Design.v

```
module simple_circuit (A, B, C, D);  
    output D; input A, B, C;  
    wire w1, w2, w3;  
    and G1 (w1, C, B);  
    or G2 (w2, A, w1);  
    and G3 (w3, A, B);  
    or G4 (D, w3, w2);  
endmodule
```

Testbench.v

```

module tb_simple_circuit;
  wire D;
  reg A, B, C;

  simple_circuit M1(A, B, C, D);

  initial begin
    A = 1'b0; B = 1'b0; C = 1'b0; #20;
    A = 1'b0; B = 1'b0; C = 1'b1; #20;
    A = 1'b0; B = 1'b1; C = 1'b0; #20;
    A = 1'b0; B = 1'b1; C = 1'b1; #20;
    A = 1'b1; B = 1'b0; C = 1'b0; #20;
    A = 1'b1; B = 1'b0; C = 1'b1; #20;
    A = 1'b1; B = 1'b1; C = 1'b0; #20;
    A = 1'b1; B = 1'b1; C = 1'b1; #20;
  end

  initial begin
    $monitor($time, " A=%b, B=%b, C=%b, D=%b ", A, B, C, D);
  end

  initial begin
    $dumpfile("tb_simple_circuit.vcd");
    $dumpvars(1, tb_simple_circuit);
  end
endmodule

```


Vvp o/p:

```

PS C:\Users\anu29\Course_materials\sem3\DDCO_lab\week2\circuit3> vvp test
VCD info: dumpfile tb_simple_circuit.vcd opened for output.
      0 A=0, B=0, C=0, D=0
     20 A=0, B=0, C=1, D=0
     40 A=0, B=1, C=0, D=0
     60 A=0, B=1, C=1, D=1
     80 A=1, B=0, C=0, D=1
    100 A=1, B=0, C=1, D=1
    120 A=1, B=1, C=0, D=1
    140 A=1, B=1, C=1, D=1

```

Gtkwave:

 

Circuit 4:

design.v

```
design.v X
6  module simple_circuit  (A, B, O, F);
5  output F;
4  input A, B, O;
3  wire w1;
2  and G1 (w1,A,B);
1  or G2 (F,w1,O);
7  endmodule
1
```

Testbench.v

```

module tb_simple_circuit;
  wire F;
  reg A, B, O;

  simple_circuit M1(A, B, O, F);

  initial begin
    A = 1'b0; B = 1'b0; O = 1'b0; #20;
    A = 1'b0; B = 1'b0; O = 1'b1; #20;
    A = 1'b0; B = 1'b1; O = 1'b0; #20;
    A = 1'b0; B = 1'b1; O = 1'b1; #20;
    A = 1'b1; B = 1'b0; O = 1'b0; #20;
    A = 1'b1; B = 1'b0; O = 1'b1; #20;
    A = 1'b1; B = 1'b1; O = 1'b0; #20;
    A = 1'b1; B = 1'b1; O = 1'b1; #20;
  end

  initial begin
    $monitor($time, " A=%b, B=%b, O=%b, F=%b ", A, B, O, F);
  end

  initial begin
    $dumpfile("tb_simple_circuit.vcd");
    $dumpvars(1, tb_simple_circuit);
  end
endmodule

```

Vvp o/p

```

< dharani@archlinux  /m/s/U/a/C/s/D/w/circuit4 ✓>
▶ vvp test
VCD info: dumpfile tb_simple_circuit.vcd opened for output.
      0 A=0, B=0, O=0, F=0
     20 A=0, B=0, O=1, F=1
     40 A=0, B=1, O=0, F=0
     60 A=0, B=1, O=1, F=1
     80 A=1, B=0, O=0, F=0
    100 A=1, B=0, O=1, F=1
    120 A=1, B=1, O=0, F=1
    140 A=1, B=1, O=1, F=1

```

Gtkwave:

