



Team DDCO

◀ ◻ ▶ ◀ ◻ ◻ ▶ ◀ ≡ ▶ ◀ ≡ ▶ ≡ ↺ 🔍 ↻

DIGITAL DESIGN AND COMPUTER ORGANIZATION



Decoders

Department of Computer Science and Engineering


- Discrete quantities of information are represented in digital systems by binary codes.
- A binary code of n bits is capable of representing up to 2^n distinct elements of coded information
- A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines. If the n -bit coded information has unused combinations, the decoder may have fewer than 2^n outputs.
- The decoders presented here are called n -to- m -line decoders, where $m \leq 2^n$
- The name decoder is also used in conjunction with other code converters, such as a BCD-to-seven-segment decoder.

Combinational logic

Decoders

Decoders

 Black box with n input lines and 2^n output lines



Only one output is a 1 for any given input

Combinational logic

Decoders


1: 2 Decoder:

A **1-to-2 decoder** is a simple combinational logic circuit that takes **1 input** and produces **2 outputs**. It is used to activate exactly **one of the two outputs** based on the binary value of the input.

Truth table :


Input (J)	Output(O_1)	Output(O_0)
0	1	0
1	0	1

1:2 decoder logic circuit:

 

Combinational logic

Decoders

 


Truth Table:

X	Y	F ₀	F ₁	F ₂	F ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

From truth table, circuit for 2x4 decoder is:

 Note: Each output is a 2-variable minterm ($X'Y'$, $X'Y$, XY' or XY)





Combinational logic

Decoders (similar to code converter – binary to octal)

3-to-8 Binary Decoder

Truth Table:

x	y	z	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

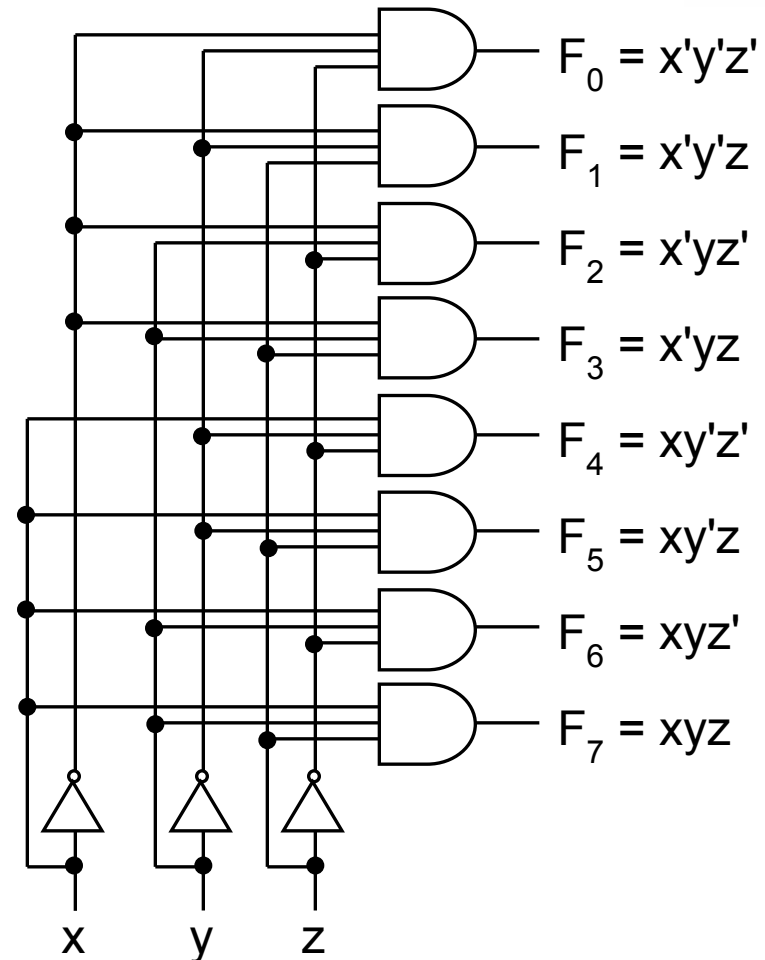 

Combinational logic

Decoders with enable input




Enable input- allows the decoders outputs to be turned “ON” or “OFF” as required. Output is only generated when the Enable input has value 1; otherwise, all outputs are 0.

Some decoders are constructed with NAND gates. Since a NAND gate produces the AND operation with an inverted output, it becomes more economical to generate the decoder minterms in their complemented form

Combinational logic

Decoders with NAND gates

 Two to four line Decoder with Enable Input



Start with a 2-bit decoder
Add an enable signal (E)

Note: use of NANDs
only one 0 active! (**active low**)
if $E = 0$

AB=10 then output is D2

E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

A decoder with enable input can function as a demultiplexer—a circuit that receives information from a single line and directs it to one of 2^n possible output lines. The selection of a specific output is controlled by the bit combination of n selection lines.


Because decoder and demultiplexer operations are obtained from the same circuit, a decoder with an enable input is referred to as a decoder – demultiplexer

Decoders with enable inputs can be connected together to form a larger decoder

Combinational logic

Decoders

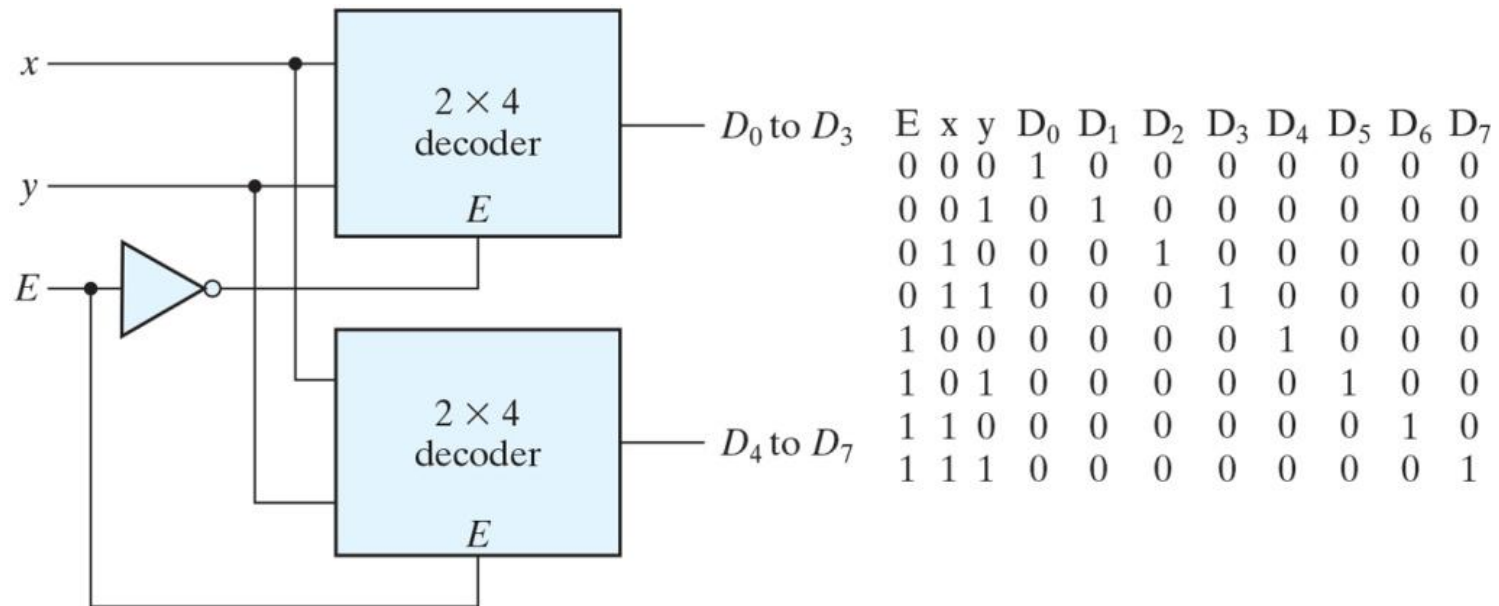
3 x 8 decoder constructed with two 2 x 4 decoders.



Combinational logic

Decoders

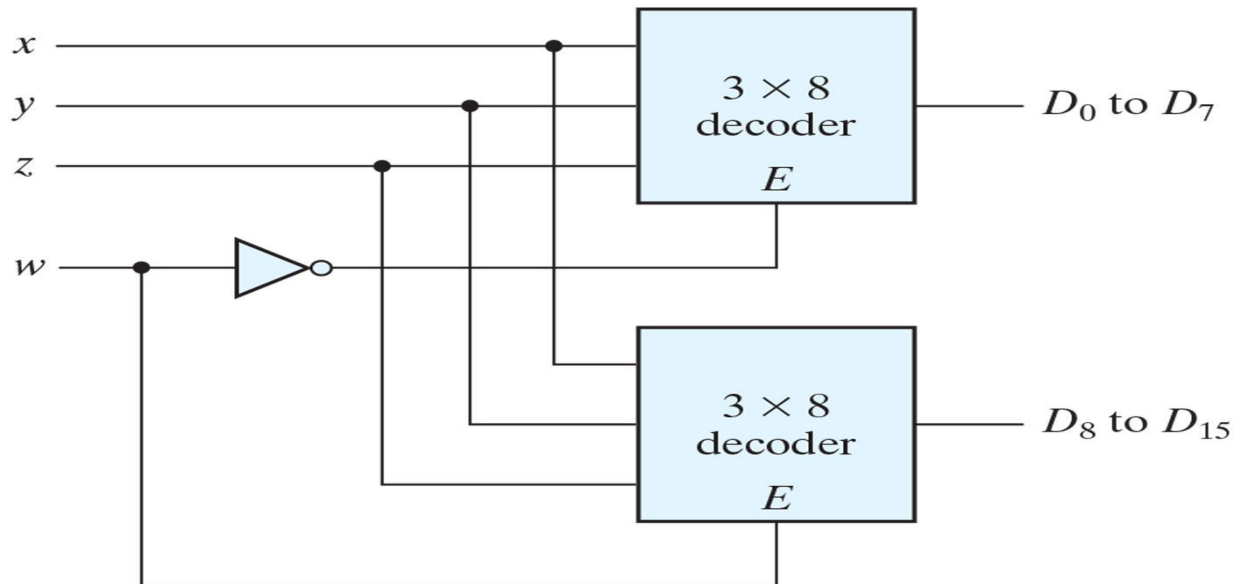4 x 16 decoder constructed with two 3 x 8 decoders.



Enable can also be active high

In this example, only one decoder can be active at a time.

x , y , z effectively select output line for w

Implementing Functions Using Decoders

Any n -variable logic function can be implemented using a single n -to- 2^n decoder to generate the minterms

- **OR gate forms the sum.**
- **The output lines of the decoder corresponding to the minterms of the function are used as inputs to the or gate.**

Any combinational circuit with n inputs and m outputs can be implemented with an n -to- 2^n decoder with m OR gates.

Suitable when a circuit has many outputs, and each output function is expressed with few minterms.

A decoder provides the 2^n minterms of n input variables
Each asserted output of the decoder is associated with a unique pattern of input bits.

Since any Boolean function can be expressed in sum-of-minterms form, a decoder that generates the minterms of the function, together with an external OR gate that forms their logical sum, provides a hardware implementation of the function.

In this way, any combinational circuit with n inputs and m outputs can be implemented with an n -to- 2^n -line decoder and m OR gates.

Questions:

1. Build XNOR Gate with 2 inputs using Decoders.
2. Implement full adder using decoders

Combinational logic

Decoders-Combinational Logic implementation


A decoder provides the 2^n minterms of n input variables
Implementation of a full adder with a decoder.

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full adder

$$S(x, y, z) = \sum (1, 2, 4, 7)$$

$$C(x, y, z) = \sum (3, 5, 6, 7)$$

 

A function with a long list of minterms requires an OR gate with a large number of inputs.

A function having a list of k minterms can be expressed in its complemented form F' with $2^n - k$ minterms.

If the number of minterms in the function is greater than $2^{n/2}$, then F' can be expressed with fewer minterms.

(Example: For 3 variables ($n=3$), total = 8 minterms.

If $F = 6$ minterms, better to write

$$F' = (\sum 6 \text{ minterms}) = (\sum \text{ of all } 8 - 6) = \text{complement of } 2 \text{ minterms}$$
$$F = (\sum 6 \text{ minterms}) = (\sum \text{ of all } 8 - 6) = \text{complement of } 2 \text{ minterms.}$$

In such a case, it is advantageous to use a NOR gate to sum the minterms of F .

Combinational logic

Decoders-Application

To manage traffic at a **4-way intersection** (North, South, East, West) **efficiently using fewer control lines**, by using a **2-to-4 line decoder**.

Why Use a Decoder?

In a 4-way intersection:

You need to **control each direction's traffic light individually**.

Without a decoder, you'd need **4 separate control signals**, one for each direction.

A **2-to-4 decoder** allows you to **use only 2 input lines** to control 4 outputs, reducing hardware complexity

Combinational logic

Decoders-Application

Understanding the 2-to-4 Decoder

Inputs: 2 bits (say A and B)

Outputs: 4 lines: Y0, Y1, Y2, Y3

Operation: When inputs = 00, output Y0 is active (others inactive)

When inputs = 01, output Y1 is active

When inputs = 10, output Y2 is active

When inputs = 11, output Y3 is active

Decoder Output	Controls Traffic Light at
Y0	North direction
Y1	South direction
Y2	East direction
Y3	West direction

Combinational logic

Decoders-Think about it

1. Build XNOR gate using Decoder
2. A function with more than $2^n/2$ minterms is better implemented using:
 - (A) A single AND gate
 - (B) Complemented function and a NOR gate
 - (C) Only XOR gates
 - (D) Full adders
3. In a 2-to-4 decoder with an active-low enable input, what happens when the enable input is 1?
 - (A) All outputs are enabled
 - (B) Decoder functions normally
 - (C) All outputs are 0
 - (D) All outputs are 1

Combinational logic

Decoders-Think about it

1. Build XNOR gate using Decoder

2. A function with more than $2^n/2$ minterms is better implemented using:

- (A) A single AND gate
- (B) Complemented function and a NOR gate
- (C) Only XOR gates
- (D) Full adders

Answer: (B)

3. In a 2-to-4 decoder with an active-low enable input, what happens when the enable input is 1?

- (A) All outputs are enabled
- (B) Decoder functions normally
- (C) All outputs are 0
- (D) All outputs are 1

Answer: (D)



THANK YOU

Team DDCO

Department of Computer Science