



DIGITAL DESIGN AND COMPUTER ORGANIZATION

Synchronous Counters

Team DDCO

Department of Computer Science and Engineering

Synchronous Counter(T1-section 6.4)


Synchronous counters are different from ripple counters in that clock pulses are applied to the inputs of all flip-flops. **A common clock triggers all flip-flops simultaneously, rather than one at a time in succession as in a ripple counter.**

The decision whether a flip-flop is to be complemented is determined from the values of the data inputs, such as T or J and K at the time of the clock edge. If $T = 0$ or $J = K = 0$, the flip-flop does not change state. If $T = 1$ or $J = K = 1$, the flip-flop complements


Counters -Recap

Incrementing Counters- Example- count number of people entering a mall


- How to store n -bits? n -bit register

 

 - How to increment an n -bit number? n -bit incrementer




- Half adder logic circuit:

 

COUNTERS

Incrementing Counters

4-Bit Incrementing Counter

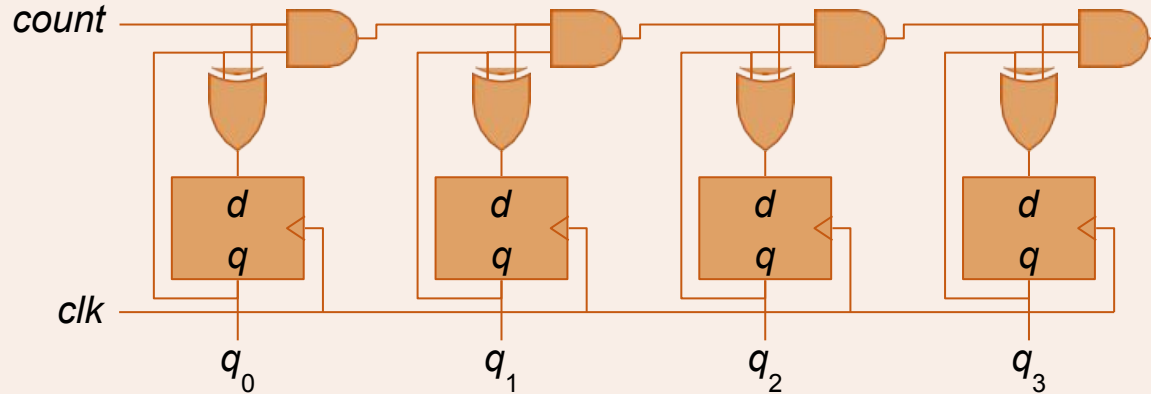


Counters Recap –Decrementing counters

- An n -bit counter that counts back from $2^n - 1$ to 0 (and back to $2^n - 1$)


Ex: a 2-bit counter, counts 11, 10, 01, 00, 11, 10,

- How to store n -bits? n -bit register

 


Parking lot counter: Starts at 20 and decrements by 1 for each car entering, displaying remaining slots until it reaches 0 → “Parking Full.”

 - How to decrement an n -bit number? n -bit decrementer




- Half Subtractor Logic Circuit:

 

COUNTERS

4-bit Decrementing Counters

4-Bit Decrementing Counter

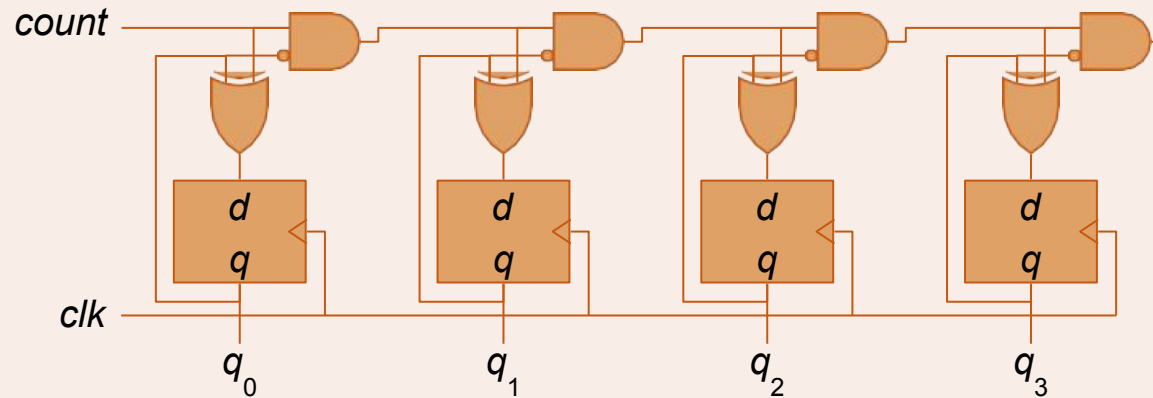

Synchronous Counters


Binary Counters

In a synchronous binary counter, the flip-flop in the least significant position is complemented with every pulse. A flip-flop in any other position is complemented when all the bits in the lower significant positions are equal to 1. For example, if the present state of a four-bit counter is $A_3A_2A_1A_0 = 0011$, the next count is 0100. A_0 is always complemented. A_1 is complemented because the present state of $A_0 = 1$. A_2 is complemented because the present state of $A_1A_0 = 11$. However, A_3 is not complemented, because the present state of $A_2A_1A_0 = 011$, which does not give an all-1's condition.

The synchronous counter can be triggered with either the positive or the negative clock edge.

Synchronous Counters

Figure 6.12
Four-bit
synchronous
binary counter.

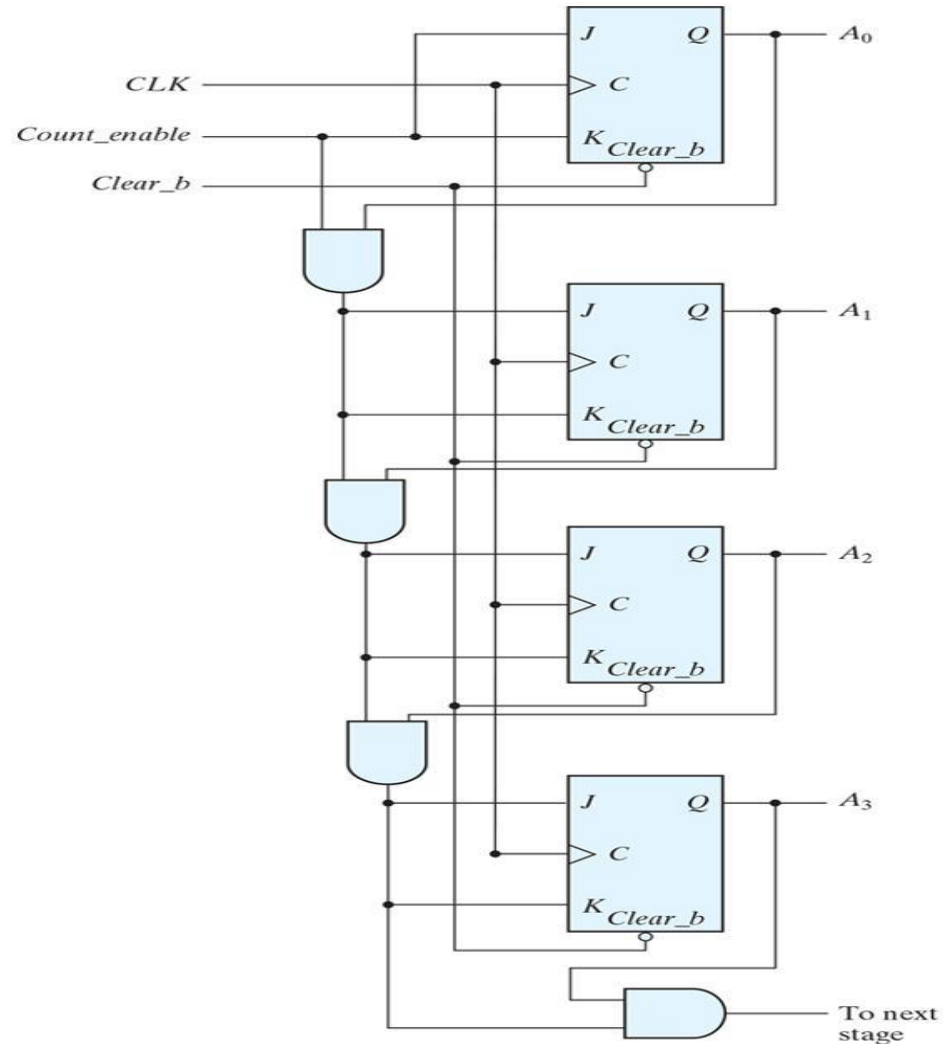

Synchronous Counters

The C inputs of all flip-flops are connected to a common clock. The counter is enabled by Count_enable. **If the enable input is 0, all J and K inputs are equal to 0 and the clock does not change the state of the counter.** The first stage, A0, has its J and K equal to 1 if the counter is enabled. The other J and K inputs are equal to 1 if all previous least significant stages are equal to 1 and the count is enabled. The chain of AND gates generates the required logic for the J and K inputs in each stage. **The counter can be extended to any number of stages, with each stage having an additional flip-flop and an AND gate that gives an output of 1 if all previous flip-flop outputs are 1.**

Synchronous Counters

Steps to design the counter using flipflops:

1. Decide the number of flipflop
2. Use excitation of the flipflop
3. State table and ckt excitation table
4. Obtain simplified equation using K map
5. Draw the sequential ckt

<https://www.tutorialspoint.com/digital-electronics/design-of-synchronous-counter.htm>

Synchronous Counters

Design 2 bit up synchronous counter using JK flipflop:
Also called Mod 4 counter

Synchronous Counters

Present (Q1 Q0)	Next (Q1 ⁺ Q0 ⁺)
00	01
01	10
10	11
11	00

Excitation table

Q(n)	Q(n+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Synchronous Counters

Present (Q1 Q0)	Next (Q1 ⁺ Q0 ⁺)	inputs			
		J1	K1	J0	k0
00	01	0	X	1	X
01	10	1	x	x	1
10	11	x	0	1	X
11	00	x	1	x	1

Excitation table

Q(n)	Q(n+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Solving using 2 variable K map of present state


$$J0 = 1, K0 = 1$$

$$J1 = Q0, K1 = Q0$$

Synchronous Counters

$J0 = 1, K0 = 1$

$J1 = Q0, K1 = Q0$

 

Synchronous Counters

Additional questions/assignment:

1. Design 2 bit synchronous down counter using JK flipflop
2. Design 3 bit synchronous down counter using T flipflop

BCD Counter.

A BCD counter counts in binary-coded decimal from 0000 to 1001 and back to 0000. Because of the return to 0 after a count of 9, a BCD counter does not have a regular pattern, unlike a straight binary count. To derive the circuit of a BCD synchronous counter, it is necessary to go through a sequential circuit design procedure.

BCD Counters o decade counter

Present State				Next State				Output	Flip-Flop Inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	T_{Q8}	T_{Q4}	T_{Q2}	T_{Q1}
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

Table 6.5

State Table for BCD Counter.

$$T_{Q1} = 1$$


$$T_{Q2} = Q_8'Q_1$$

$$T_{Q4} = Q_2Q_1$$

$$T_{Q8} = Q_8Q_1 + Q_4Q_2Q_1$$

$$y = Q_8Q_1$$

Binary Counter with Parallel Load

 

Count/Load: A control input that selects whether the counter should count or load data. If Count is active, the counter increments based on the clock. If Load is active, a 4-bit value is loaded into the counter.

Data_in (4 lines): This provides the data to be loaded into the 4-bit counter when the Load signal is active.

A_count (4 lines): The 4-bit output that holds the current count of the counter.

Clear: Resets the counter to zero.

CLK: The clock signal that controls the counting operation.


C_out: A carry-out signal that goes high when the counter overflows (from 15 back to 0).

Binary Counter with Parallel Load


Table 6.6
Function Table for the Counter of Fig. 6.14.

Clear_b	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

Binary Counter with Parallel Load

 

(a) Using the load input

 

(b) Using the clear input

FIGURE 6.15

Two ways to achieve a BCD counter using a counter with parallel load

Synchronous Counters application

Example: Image Processing with Synchronous Counters

♦ Scenario

Suppose we have a grayscale image of 256×256 pixels stored in memory.

Each pixel = 1 byte, and all pixels are stored sequentially in RAM.

Pixel(0,0) → Address 0000h

Pixel(0,1) → Address 0001h...

Pixel(255,255) → Address FFFFh

How Synchronous Counter Helps?

A 16-bit synchronous counter acts as the address generator.

On each clock pulse, the counter increments → next memory address is produced instantly.

The memory outputs the pixel value at that address.

Why Synchronous Counter?

All flip-flops update together → no glitching on the address bus.

Essential for high-speed video/image systems (e.g., cameras, medical imaging, graphics cards).

A MOD-10 synchronous counter is implemented. What will be the count sequence of the counter?

- (A) 0000 to 1111
- (B) 0000 to 1001
- (C) 0001 to 1110
- (D) 0000 to 1010

A synchronous counter is designed to count in the sequence: $000 \rightarrow 010 \rightarrow 011 \rightarrow 101 \rightarrow 110 \rightarrow 000$. What is the modulus of this counter?

- (A) 3
- (B) 5
- (C) 6
- (D) 7

A MOD-10 synchronous counter is implemented. What will be the count sequence of the counter?

- (A) 0000 to 1111
- (B) 0000 to 1001
- (C) 0001 to 1110
- (D) 0000 to 1010

Answer: (B) 0000 to 1001

A synchronous counter is designed to count in the sequence: $000 \rightarrow 010 \rightarrow 011 \rightarrow 101 \rightarrow 110 \rightarrow 000$. What is the modulus of this counter?

- (A) 3
- (B) 5
- (C) 6
- (D) 7

Answer: (B) 5, The modulus (MOD-N) of a counter = number of unique states it cycles through before repeating.



THANK YOU

Team DDCO

Department of Computer Science and Engineering